ASSIGNMENT IILP 2026 (YASHANK BHATT)

The circuit contains the following components:

- Push Button
- Buzzer
- Red LED
- Current-Limiting Resistors
- 5V Power Connector

